

## Operational Amplifier :- (OP AMP)

OPAMP is general purpose linear integrated circuit. It was developed by Robert Widlar in 1964. It is a direct coupled, high gain, differential input amplifier.


The term operational signifies that various mathematical operations such as addition, subtraction, integration, differentiation can be performed by using op-amp.

It can be used in →  
waveform forming  
active filters  
oscillators  
A/D and D/A converters.

### Advantages :-

- Here -ve feedback is applied so performance of the op-amp with negative feedback is controlled by the feedback elements independent of the characteristics of the transistors and other elements that constitute of the ~~amp~~ op-amp.
- Feedback elements are usually passive so ckt operation is very stable and predictable.
- IC of ~~op~~ op-amp is inexpensive and have temperature stabilization.

### Block diagram of OP-AMP :-

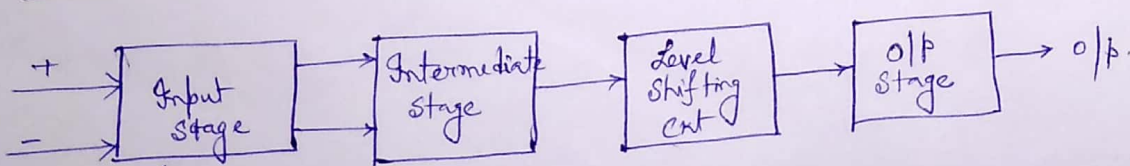

↙  
dual input, balanced output diff. amp.  
Provides most voltage gain & i/p resistance of op-amp.

- ② Dual i/p unbalanced o/p diff. amp.  
It is driven by the o/p of the 1st stage.  
It provides dc voltage well above ground level.
- ③ Emitter follower ckt to shift dc level at the o/p of the intermediate stage downward to zero volt w.r to ground.
- ④ Push pull complementary amplifier.  
Increases o/p voltage swing, current supplying capability of op-amp ↑  
It provides low o/p resistance.