
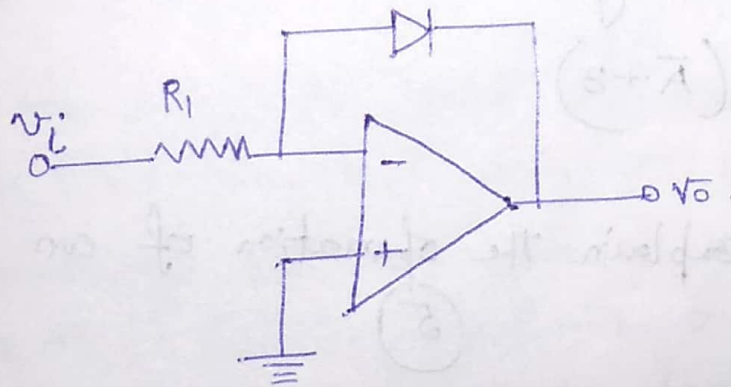


2012

- ① Discuss the operation of op-amp as an integrator. (5)
- ② (a) Implement the function $F = \overline{(AB + CD)}$ using NAND gates.
(b) $(11011)_2 = (?)_{10}$. (5)
- ③ (a) What is virtual ground of an op-amp. (2)
(b) Draw and explain the voltage comparator ckt using op-amp. (3)
- ④ (a) If the feedback resistance R_f is replaced by a diode for a negative feedback amplifier using op-amp. then derive the expression of o/p voltage v_o for it. Also mention the type of application for this modification. (5)

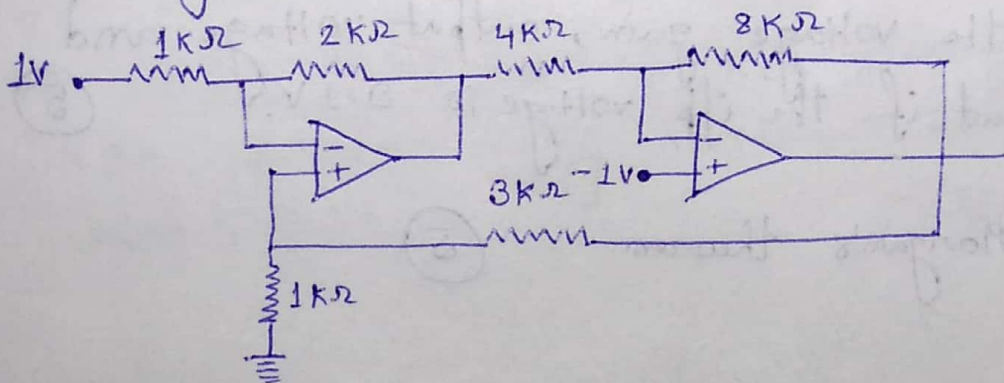

- (b) For the given ckt find the output voltage v_o . (5)



- 5+5
- ⑤ Short notes :-
- (a) Summing amplifier
 - (b) Design of EX-OR gate.

2013

- ⑥ What is an op-amp? Mention the properties of an ideal op-amp. What is type of feedback is used in an op-amp adder? (5)

⑦ (a) Perform the following number conversions :-

(i) $(10110.1101)_2 = (?)_{10}$

(ii) $(143.3125)_{10} = (?)_2$

- ⑧ Realize the Boolean expression using minimum number of NOR gates. (2)

$$Y = (A + \bar{B})(\bar{A} + B)$$

- ⑨ (a) Draw and explain the operation of an op-amp integrator ckt. (5)

- (b) An inverting amplifier has $R_f = 500 \text{ K}\Omega$, $R_i = 5 \text{ K}\Omega$. Determine the voltage gain, output voltage and input current if the i/p voltage is 0.1 V . (5)


- ⑩ SN De Morgan's theorem. (5)

2014

- ① Identify the ckt and find out the o/p voltage v_o of the ckt. ⑤

$$V_{in} = 5 \sin 2000\pi t \text{ mV.}$$
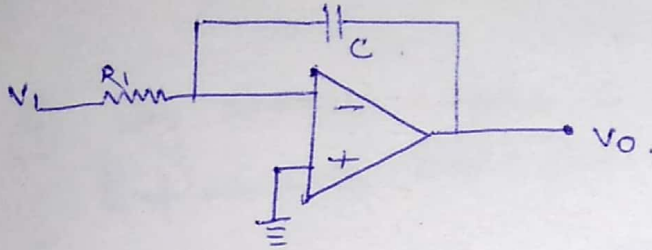
$$R = 100 \text{ k}\Omega, \quad C = 1 \text{ }\mu\text{F.}$$



② (a) $(ABC)_{10} = (?)_2$

(b) $(195)_8 = (?)_2$

- (c) realize the boolean expression using minimum no. of NAND gate.

$$Y = (A+B)(\bar{A}+\bar{B})$$

- ③ (a) What are integrator and differentiator? Describe it with suitable block diagram. ⑤

- (b) The midrange open loop gain of a certain op-amp is 120 dB. Negative feedback reduces this gain by 50 dB. What is the close loop gain. ⑤

- ④ (a) Define truth table of XOR gate. Implement XOR operation using minimum no of 2 input NAND gate. 4+1

(b) If in an adder 3 input resistances are $2k\Omega$, $4k\Omega$ and $8k\Omega$. and the feedback resistance is $10k\Omega$. What is the o/p voltage. (5)

Short note

- (5) (a) Universal gates.
(b) Operational amplifier

2015

(1) Draw the block diagram of an op-amp. and write down the characteristics of an ideal op-amp. (5)


(2) (a) $(11011 \cdot 1010)_2 = (?)_{10}$

(b) $(756 \cdot 603)_8 = (?)_{16}$

(3) (c) Realize the boolean expression using minimum no of NOR gates

$$Y = (AB' + A'B)$$

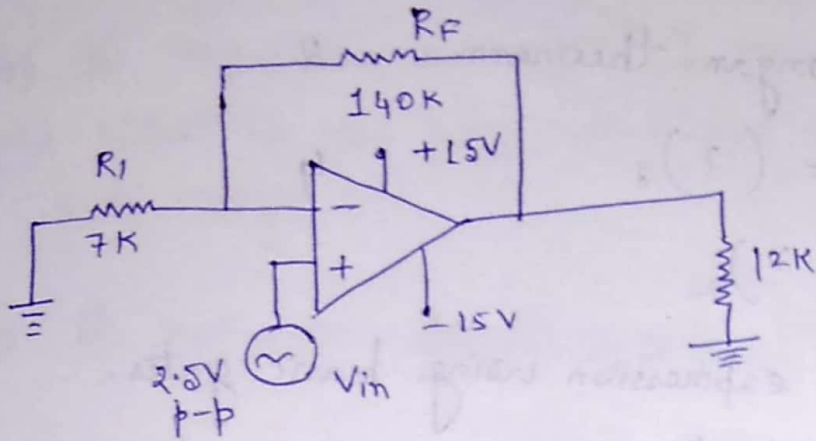
(3) Obtain the closed loop gain, CMRR in dB and maximum operating freq for the non inverting amplifier shown in fig whose common mode gain is 0.003 and Slew rate is $0.2V/\mu s$.



④ Why NAND gate is called universal gate? Explain with examples. (5)

⑤ Short Notes :- (5)
op-amp as an integrator.

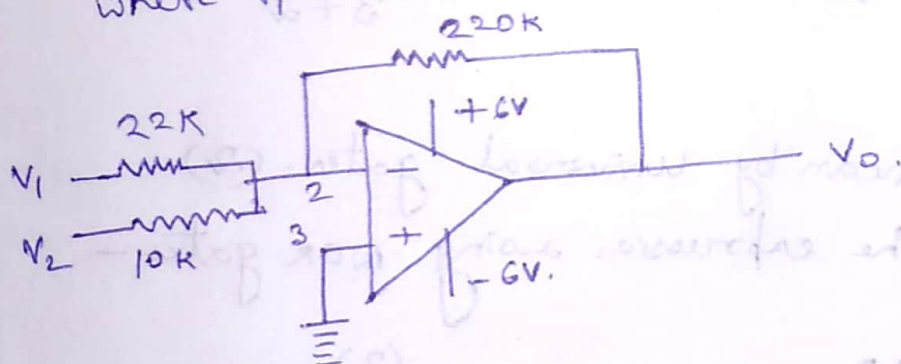2016. Identify the ext and calculate the o/p voltage. when $V_1 = 350\text{mV}$ and $V_2 = 200\text{mV}$. (1+4)



②(a) Perform the following no conversions :- (3)

(i) $(456)_{16} = (?)_8$

(ii) $(1010101)_2 = (?)_{16}$

(b) Realize the boolean expression using minimum no of NAND gates. (2)

$$Y = (A+B)(\bar{A}+B)$$

② (a) Write down De Morgan theorem. 2.

(b) (i) $(11001.101)_2 = (?)_8$ 4

(ii) $(284.56)_{10} = (?)_2$

(c) Realize the boolean expression using basic gates.

$$Y = B(\bar{A}C + A\bar{C}) + A\bar{B}C.$$

③ Short Notes:-

(a) Summing amplifier

(b) Race around condⁿ in JK latch.

2017

1. • mention the difference b/w ideal and practical op-amp. What do you mean by virtual ground of an op-amp. 3+2

2. (a) What do you mean by universal gates. (2)

(b) ~~Real~~ Realize the expression using NOR gates -

$$Y = \bar{A}\bar{B} + AB.$$

③ (a) Design an adder circuit using op-amp. to get the output expression as -

$$V_{out} = V_1 + 10V_2 + 100V_3$$

where V_1, V_2 and V_3 are i/p s of \rightarrow the op-amp and $R_F = 100K$. (3)

~~(4)~~ (b) How can an op-amp be used as an integrator. (4)

(c) What is an integrator ckt.? What are its advantages. (1+2)

(4) Sh. note \rightarrow See Morgan's theorem.

Integrated ckt (Introduction)

op-amp and its terminal properties.

Application

- (i) Inverting & Non inverting
- (ii) Adder
- (iii) Subtractor
- (iv) Constant gain amplifier
- (v) Voltage follower
- (vi) Comparator
- (vii) Integrator
- (viii) Differentiator

Logic gates and function realization with op-amps.